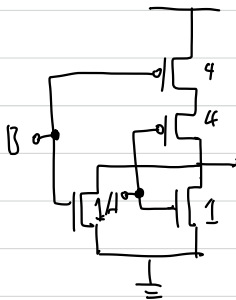


1, 4, 9, 10, 11
1, 4, 5, 6

HW#6

20175030 김민

4.1 2-in NOR.




PUN: $2R \times 2 = 4R$.

PDN: worst = R .


$\frac{4R}{k_p} = \frac{R}{k_n}$, $\therefore k_p = 4, k_n = 1$.

i) t_{pdr}

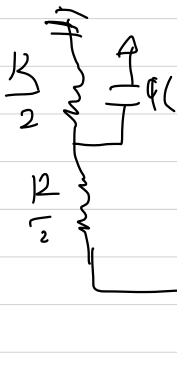

$\therefore t_{pdr} = R \cdot 4C + R(shC + 6C)$
 $= RC(10 + 5h)$

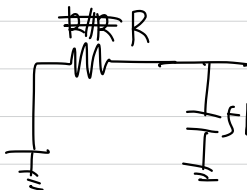ii) t_{pdf} (worst case R (H) on \uparrow)




$\therefore t_{pdf} = RC(6 + 5h)$

4.4

$\frac{2R \cdot n}{k_p} = \frac{R}{k_n}$, $k_p = 2n$, $k_n = 1$.

$\frac{n(n-1)}{2} \cdot 2RC$

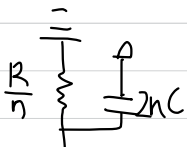

$\therefore t_{pd} = 2nC \left(\sum_{i=1}^{n-1} \frac{R}{n} \cdot i \right) + 3nRC$

$= n(n-1)RC + 3nRC$

$= (n^2 + 2n)RC$

$\frac{1}{2} 2nC + nC = 3nC$
 $\frac{1}{2} 2nC = nC$

4.9



$\frac{2R}{k_p} = \frac{4R}{k_n}$, $k_p = 2, k_n = 4$

$f_i = \frac{C_{in, gate}}{C_{in, inverter}} = \frac{6RC}{3RC} = \frac{6}{3}$

$(f = 6RH = \pi f_i)$

4.10

$D = D_p + P = \sum f_i + \sum p_i$

Each inputs will experience a inverter, so we have to compare the NAND(a), NOR(b) stages. Their parasitic cap is same to 2, but the logical effort of NOR is bigger than NAND.

\therefore (a) will be faster than (b)

(a) $G = \pi g_i = \frac{4}{3} \cdot 1 = \frac{4}{3}$, $B = 1$, $H = \frac{6C}{C} = 6$.

$\therefore f(\text{path effort}) = 6 \cdot H \cdot B = 8$

$D = \sum f_i + \sum p_i = [2 \cdot \sqrt{8} + (1+2)] \cdot \frac{1}{2} \cdot [4 \cdot 1 \cdot 4 + 3] = 8.6 \tau$

$\therefore f_i = g_1 h_1$, $\frac{6C}{x} = f$, $x = \frac{6C}{2\sqrt{2}} \approx 2.14 C$

(b) $G = \pi g_i = 1 \cdot \frac{5}{3} = \frac{5}{3}$, $B = 1$, $H = 6$.

$f = \frac{5}{3} \times 6 = 10$, $f_i = \sqrt{10} \approx 3.2$

$D = (3 \cdot 2 \times 2 + 3) \cdot \tau = 9.4 \tau$

$\therefore f_i = \frac{5}{3} \cdot \frac{3C}{2} = \frac{5C}{2}$, $y = \frac{10C}{f_i} = \sqrt{10}C = 3.2C$

4.1)

(a) $G = \frac{1}{3} \times 1 = \frac{1}{3}$, $P = 6+1=7$,
 $D = 2\sqrt{\frac{2}{3}H} + 7$

(b) $G = \frac{5}{3} \times \frac{5}{3} = \frac{25}{9}$, $P = 5$,
 $D = 2\sqrt{\frac{5}{3}H} + 5$

(c) $G = \frac{4}{3} \times \frac{7}{3}$, $P = 5$,
 $D = \frac{2}{3}\sqrt{28H} + 5$

(d) $G = \frac{5}{3} \times 1 \times \frac{4}{3}$, $P = 3+1+2+1=7$,
 $D = 4\left(\frac{20}{9}H\right)^{\frac{1}{4}} + 7$

H=1	H=5	H=20
10.3	14.3	21.6
8.3	12.5	19.9
8.5	12.9	20.8
11.8	14.3	17.3

\therefore For $H=1, 5$, (b) is fastest,
 for $H=20$, (d) is fastest. (\because more stages)

5.1

$p_{\text{switch}} = \alpha C V_{\text{DD}}^2 f$, $\alpha=0.1$, $C=450 \times 10^{-15}$ p.

$= 0.1 \times 450 \times 10^{-15} \times 0.9^2 \times 450 \times 10^6$

$\approx 1.148 \text{ W}$

5.4

$\alpha := (\text{portion of transition}) \times P = \frac{1}{10} \times \frac{1}{2} = 0.2$

5.5

2 stage will consume smallest power

(\because The least switching is 2)

The required delay is determined.

\Rightarrow Get $D_P = \sum f_i = \prod g_i h_i$ (not $(GBH)^* = f_i$)

$\therefore D = 1 \cdot \frac{1}{T} + 1 \cdot \frac{64}{x} + 2 = 20$,

$x^2 - 18x + 64 = 0$, $x = 4.88$

5.6

i) 2 stages.

$\frac{x}{1} + \frac{500}{x} + 2 = 30$, $x^2 - 28x + 500 = 0$

$b^2 - 4ac = 196 - 500 < 0$.

\therefore To fit those conditions with 2 stages is impossible

ii) 3 stages.

$\frac{x}{1} + \frac{y}{x} + \frac{500}{y} = 30$, $\min(1+x+y)$

$\Leftrightarrow x^2 + \left(\frac{500}{y} - 30\right)x + y = 0$, let $f(x,y) = 1+x+y$.

express y in function of x , and use matlab , 'fminbnd' ($-f(x,y)$)

Then, for $x=5$, $y=32.09$, energy = 38.09

iii) 4 stages.

$\frac{x}{1} + \frac{y}{x} + \frac{z}{y} + \frac{500}{z} = 30$, $\min(1+x+y+z)$

Solve in same way,

for, $x=2.15$, $y=6.23$, $z=31.43$, energy = 37.8

from i), ii), iii), 3 stage has least power