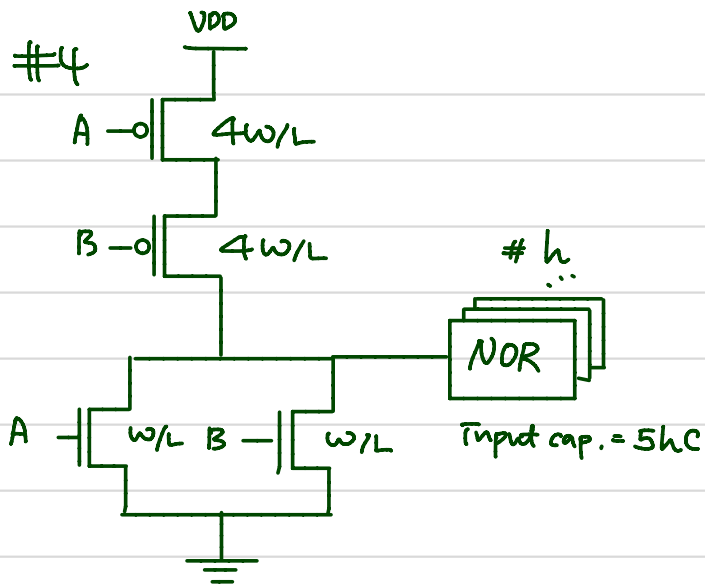


Digital I.C


Assignment

20191009 Inho Jung






① rising delay


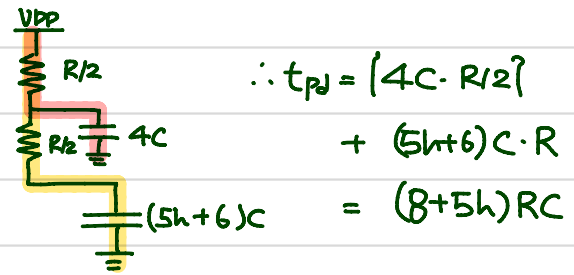


② falling delay

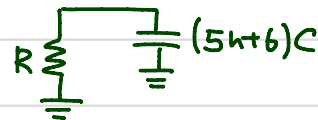


$$t_{pd} = (5h+6)RC$$

#4.4 n Input NOR gate.

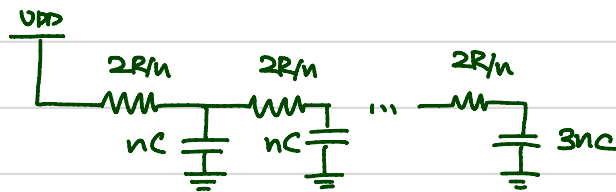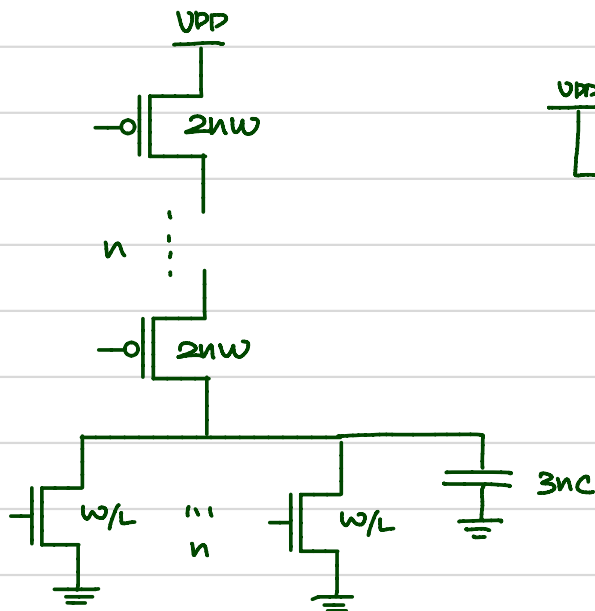

$$\frac{2R}{n} \cdot nC + 2 \cdot \frac{2R}{n} \cdot nC + \dots + (n-1) \cdot \frac{2R}{n} \cdot nC + \frac{2R}{n} \cdot n \cdot 3nC = (n^2 + 2n)RC$$

#4.9

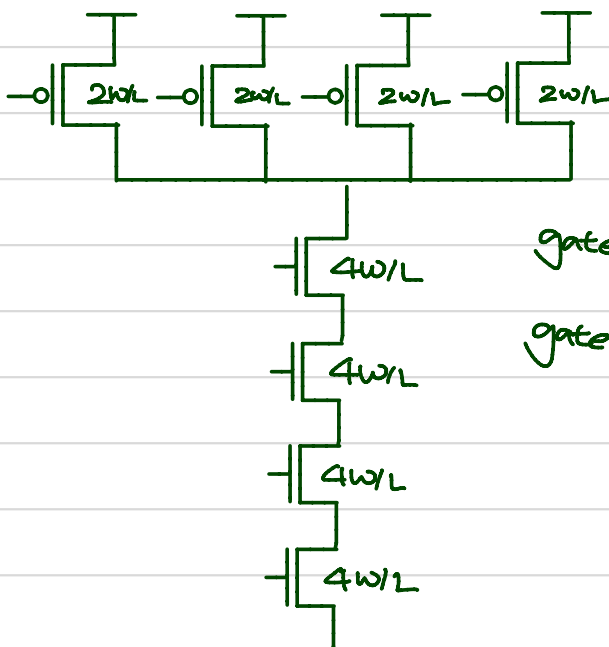

$$\text{gate capacitance} = 2C + 4C = 6C$$

$$\text{gate cap. of standard inverter} = 2C + C = 3C$$

$$\therefore \text{logical effort} = 6C/3C = 2$$

#4.10


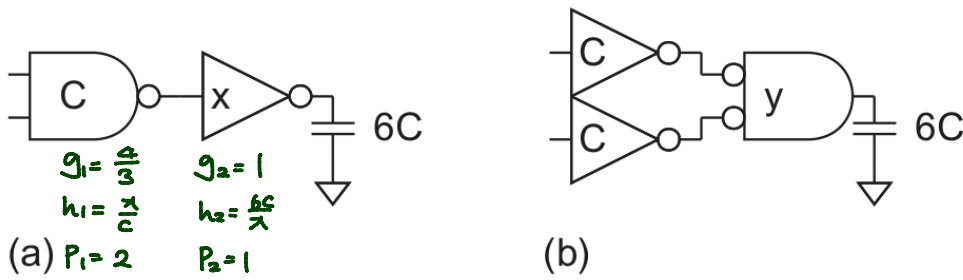


FIGURE 4.39 2-input AND gate

$$a) \quad g_1 h_1 = g_2 h_2 = (g_1 g_2 h_1 h_2)^{1/2} = \frac{4}{3} \cdot 1 \cdot \frac{x}{2} \cdot \frac{6C}{x} = (8)^{1/2} = 2\sqrt{2}$$
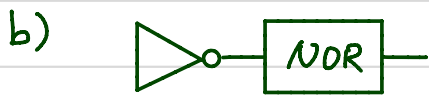
$$\therefore \text{Delay} = g_1 h_1 + P_1 + g_2 h_2 + P_2 = 2\sqrt{2} + 2 + 2\sqrt{2} + 1 = 3 + 4\sqrt{2} = 8.6$$



$$g_1 = 1 \quad g_2 = 5/3$$

$$h_1 = y/C \quad h_2 = 6C/y$$

$$P_1 = 1 \quad P_2 = 2$$





$$g_1 h_1 = g_2 h_2 = (g_1 h_1 g_2 h_2)^{1/2} = 10^{1/2}$$

$$\text{delay} = g_1 h_1 + P_1 + g_2 h_2 + P_2$$

$$= 2\sqrt{10} + 3 = 3.16 \times 2 + 3 = 9.32$$

$\therefore \text{delay (a)} < \text{delay (b)}$

#4.11

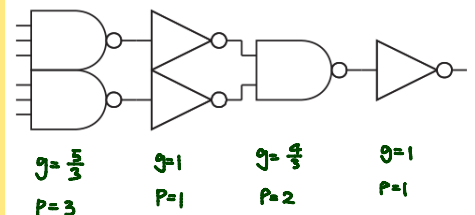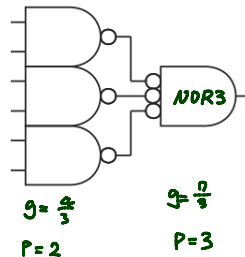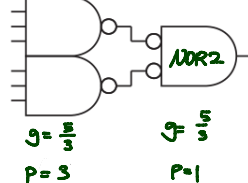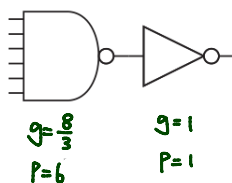

$$H=1 \quad 2 \cdot \left(\frac{8}{3} \cdot 1\right)^{1/2} + \eta = 10.3 \quad 2 \cdot \left(\frac{5}{3} \cdot \frac{5}{3}\right)^{1/2} + 4 = 8.3 \quad 2 \cdot \left(\frac{4}{3} \cdot \frac{4}{3}\right)^{1/2} + 5 = 8.5 \quad 4 \cdot \left(\frac{5}{3} \cdot \frac{4}{3}\right)^{1/4} + \eta = 11.8$$

$$H=5 \quad 2 \cdot \left(\frac{8}{3} \cdot 5\right)^{1/2} + \eta = 14.3 \quad 2 \cdot \left(\frac{5}{3} \cdot \frac{5}{3} \cdot 5\right)^{1/2} + 4 = 12.5 \quad 2 \cdot \left(\frac{4}{3} \cdot \frac{4}{3} \cdot 5\right)^{1/2} + 5 = 12.9 \quad 4 \cdot \left(\frac{5}{3} \cdot \frac{4}{3} \cdot 5\right)^{1/4} + \eta = 14.3$$

$$H=20 \quad 2 \cdot \left(\frac{8}{3} \cdot 20\right)^{1/2} + \eta = 21.6 \quad 2 \cdot \left(\frac{5}{3} \cdot \frac{5}{3} \cdot 20\right)^{1/2} + 4 = 19.9 \quad 2 \cdot \left(\frac{4}{3} \cdot \frac{4}{3} \cdot 20\right)^{1/2} + 5 = 20.8 \quad 4 \cdot \left(\frac{5}{3} \cdot \frac{4}{3} \cdot 20\right)^{1/4} + \eta = 17.3$$


#5.1 $P = \kappa C V^2 f = 0.1 (450 \times 10^{-12}, n_0) \cdot 0.9^2 \cdot 450 \times 10^6 = 1.08 W$

#5.4 10 cycle 동안 2번의 $0 \rightarrow V_{DD}$ transition

$\therefore 0.2$

#5.5 Switch의 개수가 가장 적은 2 stage 가 가장 적은 energy를 소비

#5.6

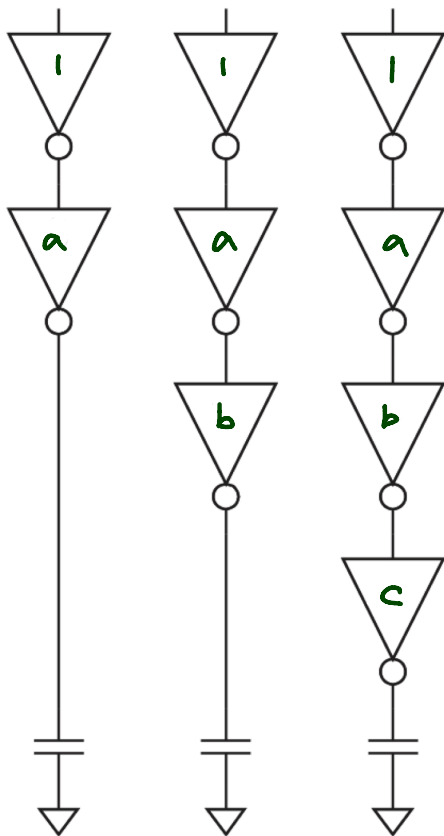

- 2stage

$$d = a + 500/a + 2$$

$$E = 1 + a$$

- 3stage

$$d = a + b/a + 500/b + 3$$

$$E = 1 + a + b$$

$$a = 5 \quad b = 32.09 \quad E = 38.09$$

- 4stage

$$d = a + b/a + c/b + 500/c + 4$$

$$E = 1 + a + b + c$$

$$a = 2.15 \quad b = 6.23 \quad c = 31.43 \quad E = 39.81$$