

---

# DIC L12: Inverter (2)

Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Lab.  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology

## 2.5. DC transfer (9)

- Input threshold,  $V_{inv}$  (or switching threshold)
  - When  $V_{in} = V_{out} = V_{inv}$
- Beta ratio
  - Skewed
    - HI-skewed,  $\frac{\beta_p}{\beta_n} > 1$ 
      - Stronger PMOS
    - LO-skewed,  $\frac{\beta_p}{\beta_n} < 1$ 
      - Weaker PMOS

 


Fig. 2.28

## 2.5. DC transfer (10)

---

- Quantitative analysis

$$I_{dn} = \frac{\beta_n}{2} (V_{inv} - V_{tn})^2$$

$$I_{dp} = -\frac{\beta_p}{2} (V_{inv} - V_{DD} - V_{tp})^2$$

- After manipulation, we have

$$V_{inv} = \frac{V_{DD} + V_{tp} + V_{tn} \sqrt{\frac{1}{r}}}{1 + \sqrt{\frac{1}{r}}} \quad \text{Eq. (2.55)}$$

- For a special case with  $r = 1$ ,  $V_{inv} = \frac{V_{DD} + V_{tn} + V_{tp}}{2}$

## 2.5. DC transfer (11)

---

- Quantitative analysis with velocity saturation

$$I_{dn} = W_n C_{ox} v_{sat-n} (V_{inv} - V_{tn})$$
$$I_{dp} = -W_p C_{ox} v_{sat-p} (V_{inv} - V_{DD} - V_{tp})$$

- After manipulation, we have

$$V_{inv} = \frac{V_{DD} + V_{tp} + V_{tn} \frac{1}{r}}{1 + \frac{1}{r}} \quad \text{Eq. (2.57)}$$


- (Here,  $r = \frac{W_p v_{sat-p}}{W_n v_{sat-n}}$ )

- For a special case with  $r = 1$ ,  $V_{inv} = \frac{V_{DD} + V_{tn} + V_{tp}}{2}$
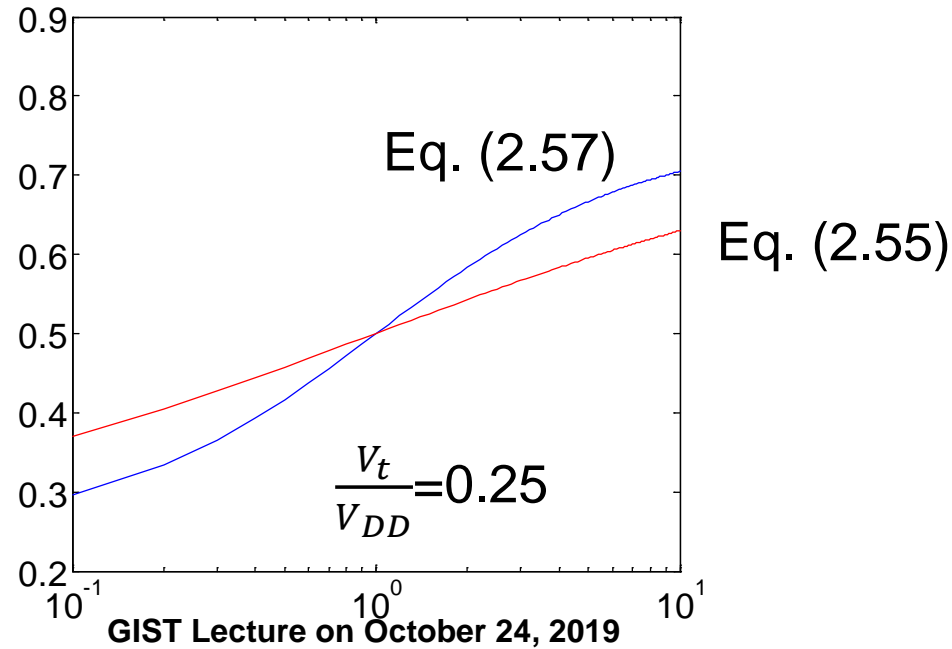
## 2.5. DC transfer (12)

---

- Eq. (2.55) and Eq. (2.57)
  - Let's draw  $\frac{V_{inv}}{V_{DD}}$  as a function of  $r$ . Assume that  $V_t = V_{tn} = -V_{tp}$ .



## 2.5. DC transfer (13)

- Noise margin

 


Fig. 2.29

## 2.5. DC transfer (12)

- Unity gain points
  - Two unity gain points
  - $V_{IL}$
  - $V_{IH}$

 


Fig. 2.30

## 2.5. DC transfer (13)

---

- Pass transistor

 
 
 
 


Fig. 2.31