
DIC L19: Delay (7)


DIC L20: Power (1)

Sung-Min Hong (smhong@gist.ac.kr)

Semiconductor Device Simulation Lab.
School of Electrical Engineering and Computer Science
Gwangju Institute of Science and Technology

4.4. Linear delay model (7)


- Example 4.10

 

- Logical Effort: $g = 1$
- Electrical Effort: $h = 4$
- Parasitic Delay: $p = 1$
- Stage Delay: $d = 5$
- When $\tau = 3RC = 3 \text{ ps}$, the total delay is 15 ps.

4.4. Linear delay model (8)


- Example 4.11

 

- Logical Effort: $g = 1$
- Electrical Effort: $h = 1$
- Parasitic Delay: $p = 1$
- Stage Delay: $d = 2$
- Frequency: $f_{\text{osc}} = 1/(2 \cdot N \cdot d) = 1/4N$

 4.5. Logical effort of paths (1)

- Multistage logic networks
 - Logical effort is independent of size.
 - Electrical effort depends on sizes.



- Some metrics for the path as a whole?

4.5. Logical effort of paths (2)

- Multistage logic networks
 - Logical effort is independent of size.
 - Electrical effort depends on sizes.

- Path logical effort $G = \prod g_i$ Eq. (4.32)

- Path electrical effort $H = \frac{C_{out-path}}{C_{in-path}}$ Eq. (4.33)

- Path effort $F = \prod f_i = \prod g_i h_i$ Eq. (4.34)

4.5. Logical effort of paths (3)

- With the branching effort, B ,

$$F = GBH$$

Eq. (4.37)

- Path effort delay

$$D_F = \sum f_i$$

- Path parastic delay

$$P = \sum p_i$$

Eq. (4.38)

- Path delay

$$D = \sum d_i = D_F + P$$

4.5. Logical effort of paths (4)

- Paths that branch

$$G = 1$$

$$H = 90 / 5 = 18$$

$$GH = 18$$

$$h_1 = (15 + 15) / 5 = 6$$

$$h_2 = 90 / 15 = 6$$

$$F = g_1 g_2 h_1 h_2 = 36 = 2GH$$

- It's not difficult to evaluate F .
 - Even without specific sizes, we can do it!
 - It means that F is fixed.

 


Fig. 4.30

4.5. Logical effort of paths (5)

- Important observation
 - We want to make D_F (a sum of f_i 's) small.
 - But, F (a product of f_i 's) is fixed.
- Assume N stages.
- Inequality of arithmetic and geometric means

$$f_1 + f_2 + \cdots + f_N \geq N \sqrt[N]{f_1 f_2 \cdots f_N}$$

- The equality holds if and only if $f_1 = f_2 = \cdots = f_N$.
- Therefore, the minimum value of D_F is given by

$$D_F = N \sqrt[N]{F}$$

4.5. Logical effort of paths (6)

- The minimum delay

$$D = NF^{1/N} + P$$

Eq. (4.40)

- This is a key result of logical effort.
- It shows that:
 - The minimum delay of the path can be estimated knowing only the number of stages (N), path effort ($F = GBH$), and parasitic delays (P) without the need to assign transistor sizes.
- When the stage effort is given as $\hat{f} = F^{1/N}$,
 - The transistor size can be determined to satisfy $\hat{f} = gh = g \frac{C_{out}}{C_{in}}$.
 - Working backward!

4.5. Logical effort of paths (7)

- Example 4.13

$$G = \frac{4}{3} \times \frac{5}{3} \times \frac{5}{3} = \frac{100}{27}$$

$$B = 3 \times 2 = 6$$

$$H = \frac{45}{8}$$

 


Fig. 4.31

4.5. Logical effort of paths (8)

- Example 4.14

$$D = N(64)^{1/N} + N$$

 


Fig. 4.33

5.1. Introduction (1)

- Definitions

- Instantaneous power

$$P(t) = I(t)V(t) \quad \text{Eq. (5.1)}$$

- Energy

$$E = \int_0^T P(t)dt \quad \text{Eq. (5.2)}$$

- Average power

$$P_{avg} = \frac{E}{T} = \frac{1}{T} \int_0^T P(t)dt \quad \text{Eq. (5.3)}$$

5.1. Introduction (2)

- Charging a capacitor

- Energy stored in the capacitor

$$\int_0^{\infty} I(t)V_{out}(t)dt = \frac{1}{2} C_L V_{DD}^2$$

- The energy delivered from the power supply

$$\int_0^{\infty} I(t)V_{DD}dt = C_L V_{DD}^2$$

- Half of the energy from V_{DD} is dissipated in the PMOS transistor as heat.

 


Fig. 5.4

5.1. Introduction (3)

- Switching waveforms

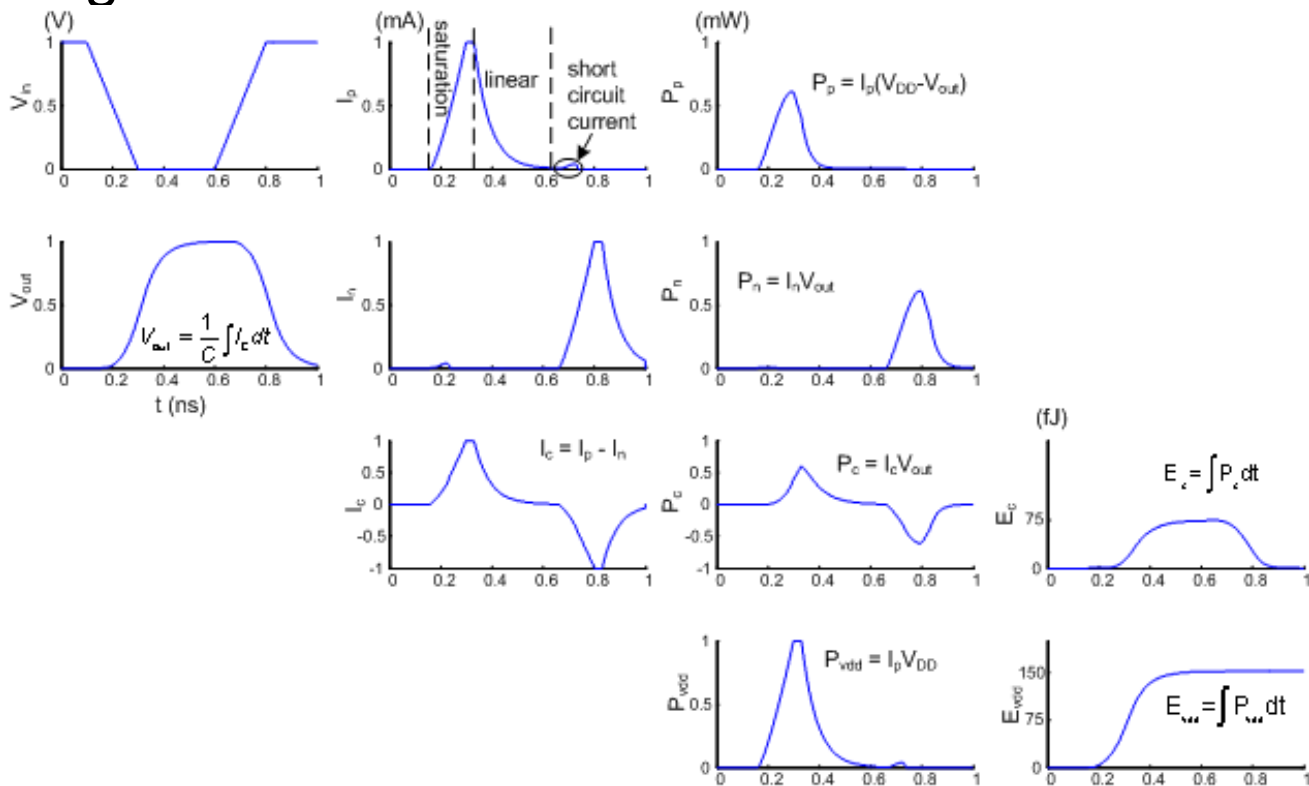


Fig. 5.5

5.1. Introduction (4)

- Average power dissipation

- When a gate is

$$P_{switching} = \frac{CV_{DD}^2}{T} = CV_{DD}^2 f_{sw}$$

- Most gates do not switch every clock cycle.

- Let $f_{sw} = \alpha f$, where α is the activity factor.

- Then, the dynamic power is written as

$$P_{switching} = \alpha CV_{DD}^2 f$$