

---

# DIC L11: Inverter (1)


Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Lab.  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology

## 2.4. Nonideal IV (12)

---

- Threshold voltage (Body effect)
  - It is given by
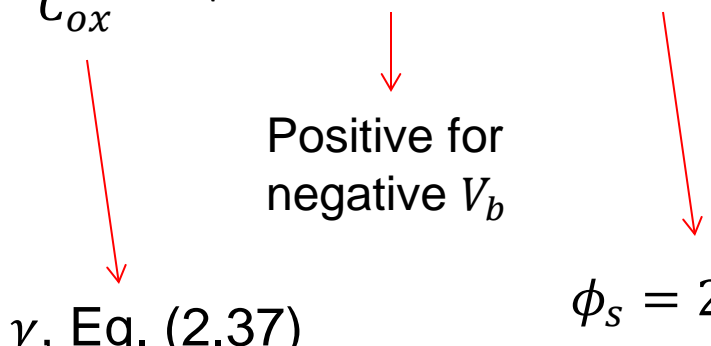
$$V_t = \frac{\sqrt{2\epsilon_{si}qN_A}}{C_{ox}} \sqrt{\phi_s + V_{sb}} + V_{FB} + \phi_s$$


Positive for  
negative  $V_b$

$\gamma$ , Eq. (2.37)

$$\phi_s = 2v_T \log \frac{N_A}{n_i}, \text{ Eq. (2.36)}$$

- Written as

$$V_t = V_{t0} + \gamma (\sqrt{\phi_s + V_{sb}} - \sqrt{\phi_s})$$

## 2.4. Nonideal IV (13)

- Leakage
  - Subthreshold slope
  - DIBL
    - Drain-induced barrier lowering
  - GIDL
    - Gate-induced drain leakage

 


Fig. 2.20

## 2.5. DC transfer (1)

- A CMOS inverter
  - The transistor is a switch with an infinite off-resistance and a finite on-resistance.


 


Fig. 2.26

 

## 2.5. DC transfer (2)


---

- Important properties (Taken from Rabaey's book)
  - The HIGH and LOW output levels equal  $V_{DD}$  and GND, respectively.
  - The logic levels are not dependent upon the relative device sizes, so that the transistors can be minimum size. (Ratioless)
  - A well-designed CMOS inverter has a low output impedance.
  - The input resistance of the CMOS inverter is extremely high.
  - The absence of current flow between  $V_{DD}$  and GND means that the gate does not consume any static power.
 
## 2.5. DC transfer (3)

---

- Intel 4004
  - In 1971, the first microprocessor was released.
  - It has about 2300 transistors.
  - It was designed by Federico Faggin.
  - Masatoshi Shima helped him.
- It was implemented in a pure NMOS tech.



(4004)

Die size: 12 mm<sup>2</sup>

Min. feature size: 10 micron


Max. clock speed: 740 kHz



Federico Faggin  
(Wikipedia)
 
## 2.5. DC transfer (4)

- NMOS
  - It is turned on at HIGH input voltages




Cutoff	Linear	Saturated
$V_{gsn} < V_{tn}$ $V_{in} < V_{tn}$	$V_{gsn} > V_{tn}$ $V_{in} > V_{tn}$ $V_{dsn} < V_{gsn} - V_{tn}$ $V_{out} < V_{in} - V_{tn}$	$V_{gsn} > V_{tn}$ $V_{in} > V_{tn}$ $V_{dsn} > V_{gsn} - V_{tn}$ $V_{out} > V_{in} - V_{tn}$

Table 2.2
 
## 2.5. DC transfer (5)

- PMOS
  - It is turned on at LOW gate voltages.




Cutoff	Linear	Saturated
$V_{gsp} > V_{tp}$ $V_{in} > V_{DD} + V_{tp}$	$V_{gsp} < V_{tp}$ $V_{in} < V_{DD} + V_{tp}$ $V_{dsp} > V_{gsp} - V_{tp}$ $V_{out} > V_{in} - V_{tp}$	$V_{gsp} < V_{tp}$ $V_{in} < V_{DD} + V_{tp}$ $V_{dsp} < V_{gsp} - V_{tp}$ $V_{out} < V_{in} - V_{tp}$

Table 2.2




## 2.5. DC transfer (6)

- Two curves are drawn together.

 
 
## 2.5. DC transfer (7)


- Same graph, but in terms of  $V_{in}$  and  $V_{out}$


 
## 2.5. DC transfer (8)

---

- Operating regions
  - We have five points. Identify the operational modes of transistors.



## 2.5. DC transfer (9)

- Input threshold,  $V_{inv}$  (or switching threshold)
  - When  $V_{in} = V_{out} = V_{inv}$
- Beta ratio
  - Skewed
    - HI-skewed,  $\frac{\beta_p}{\beta_n} > 1$ 
      - Stronger PMOS
    - LO-skewed,  $\frac{\beta_p}{\beta_n} < 1$ 
      - Weaker PMOS

