
 


Digital Integrated Circuit HW#6.
20175138 임경득

Exercise 4.1

 


$$2 \times \frac{2R}{P} = \frac{R}{n} \Rightarrow P:n = 4:1$$



gate capacitance = $5C$ (at each input)


parasitic capacitance = $C + C + 4C = 6C$

Falling propagation delay

 

$$t_{pdf} = R \times (6+5h)C = (6+5h)RC$$

Rising propagation delay

 


$$t_{pdr} = \frac{R}{2} \cdot 4C + \left(\frac{R}{2} + \frac{R}{2}\right) \times (6+5h)C = (8+5h)RC$$

Answer) $t_{pdf} = (6+5h)RC$, $t_{pdr} = (8+5h)RC$

(2-input NOR Gate is sketched above)

Exercise 4.4.

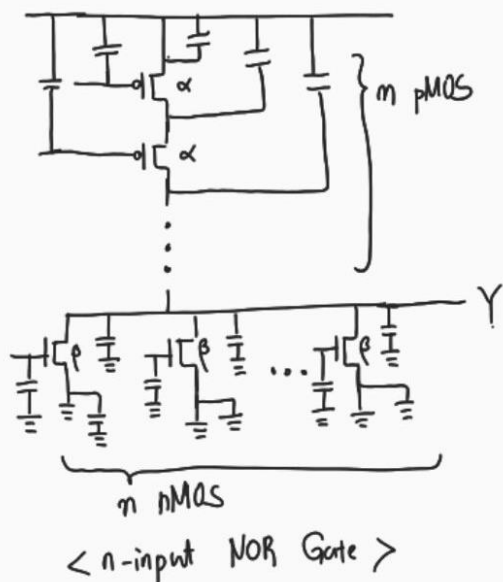

$$\frac{2R}{\alpha} \cdot n = \frac{R}{\beta} = R$$

$$\alpha = 2n, \beta = 1$$

$$\text{parasitic capacitance} = 2nC + n \times C = 3nC$$


$$t_{pd} = \sum_{i=1}^{n-1} \left(\frac{iR}{n} \right) (2nC) + 3nRC$$

$$= \sum_{i=1}^{n-1} 2iRC + 3nRC$$

$$= 2RC \cdot \frac{n(n-1)}{2} + 3nRC = (n^2 + 2n)RC$$

Answer) $t_{pd} = (n^2 + 2n)RC$

Exercise 4.9

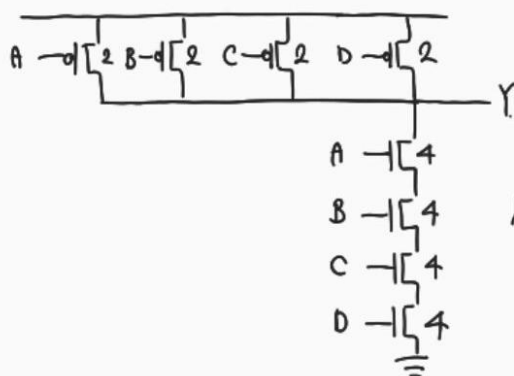

$$\text{gate capacitance} = 2C + 4C = 6C$$

logical effort, f

$$= \frac{(\text{ratio of the input capacitance})}{(\text{ratio of the input capacitance of the inverter})}$$

$$= \frac{6C}{3C} = \frac{6}{3}$$

Exercise 4.10.

(a) would be faster than (b) because NAND gate in (a) has lower logical effort than the NOR gate in (b).

$$\begin{array}{l} \text{At (a), } G = \frac{4}{3} \cdot 1 = \frac{4}{3} \\ B = 1 \\ H = 6 \end{array} \Rightarrow F = \frac{4}{3} \cdot 1 \cdot 6 = 8$$

$$D = ((2+1) + 2 \cdot 8^{\frac{1}{2}})\tau = 8.6\tau, \quad 8^{\frac{1}{2}} = \frac{6C}{x} \Rightarrow x = 2.12C$$

$$\begin{array}{l} \text{At (b), } G = 1 \cdot \frac{5}{3} = \frac{5}{3} \\ B = 1 \\ H = 6 \end{array} \Rightarrow F = \frac{5}{3} \cdot 1 \cdot 6 = 10$$

$$D = ((2+1) + 2 \cdot 10^{\frac{1}{2}})\tau = 9.3\tau, \quad 10^{\frac{1}{2}} = \frac{5}{3} \frac{6C}{y} = \frac{10C}{y} \Rightarrow y = 3.16C$$

Answer) path effort in (a) : 8 , path effort in (b) : 10 .

delay in (a) : 8.6τ , delay in (b) : 9.3τ

$x = 2.12C$, $y = 3.16C$

Exercise 4.11

	N	G	P	D (H=1)	D (H=5)	D (H=20)
(a)	2	$\frac{8}{3} \cdot 1 = \frac{8}{3}$	$1+6=7$	10.27	14.30	21.61
(b)	2	$\frac{5}{3} \cdot \frac{5}{3} = \frac{25}{9}$	$3+2=5$	8.33	12.45	19.91
(c)	2	$\frac{4}{3} \cdot \frac{2}{3} = \frac{28}{9}$	$2+3=5$	8.53	12.89	20.78
(d)	4	$\frac{5}{3} \cdot 1 \cdot \frac{4}{3} \cdot 1 = \frac{20}{9}$	$3+1+2+1=7$	11.88	14.30	19.33

Answer) At $H=1$, (b) is the fastest.

At $H=5$, (b) is the fastest.

At $H=20$, (d) is the fastest.

Exercise 5.1.

$$P = \alpha C V_{DD}^2 f = 0.1 \times 450 \times 10^{-12} \times 70 \times 0.9^2 \times 450 \times 10^6 = 1.148 \text{ W}$$

Answer) 1.148 W

Exercise 5.4.

$$\text{clock rate} = 1 \text{ GHz} \Rightarrow \text{period} = 10^{-9} \text{ s}$$

The signal makes 4 transitions in 10 cycles.

$$\alpha = \frac{1}{2} \times \frac{4}{10} = 0.2$$

Answer) 0.2

Exercise 5.5

A two stage will use the least energy.

stage	delay (=20)	Energy
2	$2 + 64/x + 1$	$1 + x \Rightarrow x = 4.88, E = 5.88$

Answer) 2 stage, transistor width = 4.88.

Exercise 5.6

stage	delay (=30)	Energy
2	$2 + x + \frac{600}{x}$	$1 + x \Rightarrow x \text{ would be imaginary number}$
3	$3 + \frac{100}{x} + \frac{x}{y} + y$	$1 + x + y \Rightarrow x = 5.00, y = 32.09 \Rightarrow E = 38.09$

Answer) 3 stage, transistor width = 5.00, 32.09.