

---

# DIC L14: Delay (2)

Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Lab.  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology

# 4.1. Introduction (1)

---


- Transient response
  - DC analysis:  $V_{out}$  if  $V_{in}$  is a constant
  - Transient analysis:  $V_{out}(t)$  if  $V_{in}(t)$  changes
  - A set of differential equations should be solved.
    - Consider a vector of state variables,  $\mathbf{x}$ .
    - In many cases,
$$\frac{d}{dt}(\mathbf{C} \mathbf{x}) + G(\mathbf{x}) = \mathbf{b}$$
  - Input is usually considered to be a step or ramp.
    - From 0 to  $V_{DD}$  or vice versa

# 4.1. Introduction (2)

$$V_{in}(t) =$$

$$V_{out}(t < t_0) =$$

$$\frac{dV_{out}(t)}{dt} =$$

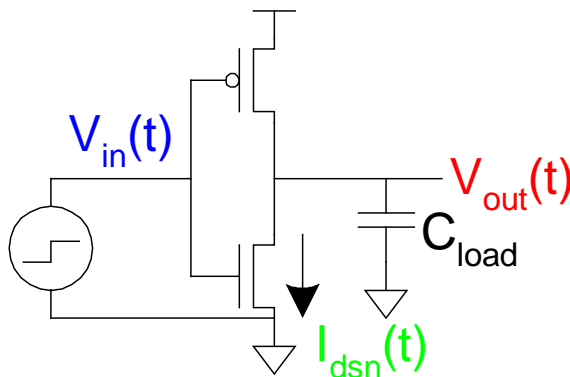

$$I_{dsn}(t) = \begin{cases} & t \leq t_0 \\ V_{out} > V_{DD} - V_t \\ V_{out} < V_{DD} - V_t \end{cases}$$

# 4.1. Introduction (3)

- Definitions

- $t_{pdr}$ : *rising propagation delay*
  - From input to rising output crossing  $V_{DD}/2$
- $t_{pdf}$ : *falling propagation delay*
  - From input to falling output crossing  $V_{DD}/2$
- $t_{pd}$ : *average propagation delay*,  $t_{pd} = (t_{pdr} + t_{pdf})/2$
- $t_r$ : *rise time*
  - From output crossing  $0.2 V_{DD}$  to  $0.8 V_{DD}$
- $t_f$ : *fall time*
  - From output crossing  $0.8 V_{DD}$  to  $0.2 V_{DD}$


 


Fig. 4.1

# 4.1. Introduction (4)

---

- Inverter example

 

## 4.3. RC delay model (1)

---

- Easily estimate the delay
- RC delay models approximate the nonlinear transistor IV and CV characteristics with an average resistance and capacitance over the switching range of the gate.
  - Total capacitance on output node:  $C$
  - Effective resistance:  $R$
  - Propagation delay  $\sim RC$
- Characterize transistors by finding their effective  $R$  values.
  - Not accurate, however good enough to predict RC delay

## 4.3. RC delay model (2)

- Equivalent RC circuits
  - Unit NMOS (for example,  $4\lambda/2\lambda$ ) is defined to have effective resistance  $R$ . An NMOS, whose width is  $k$  times unit width, has resistance  $R/k$ .
  - Let us assume that unit PMOS has effective resistance  $2R$ .

 


Fig. 4.5