

---

# DIC L13: Delay (1)

Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Lab.  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology

## 2.5. DC transfer (14)

- Noise margin

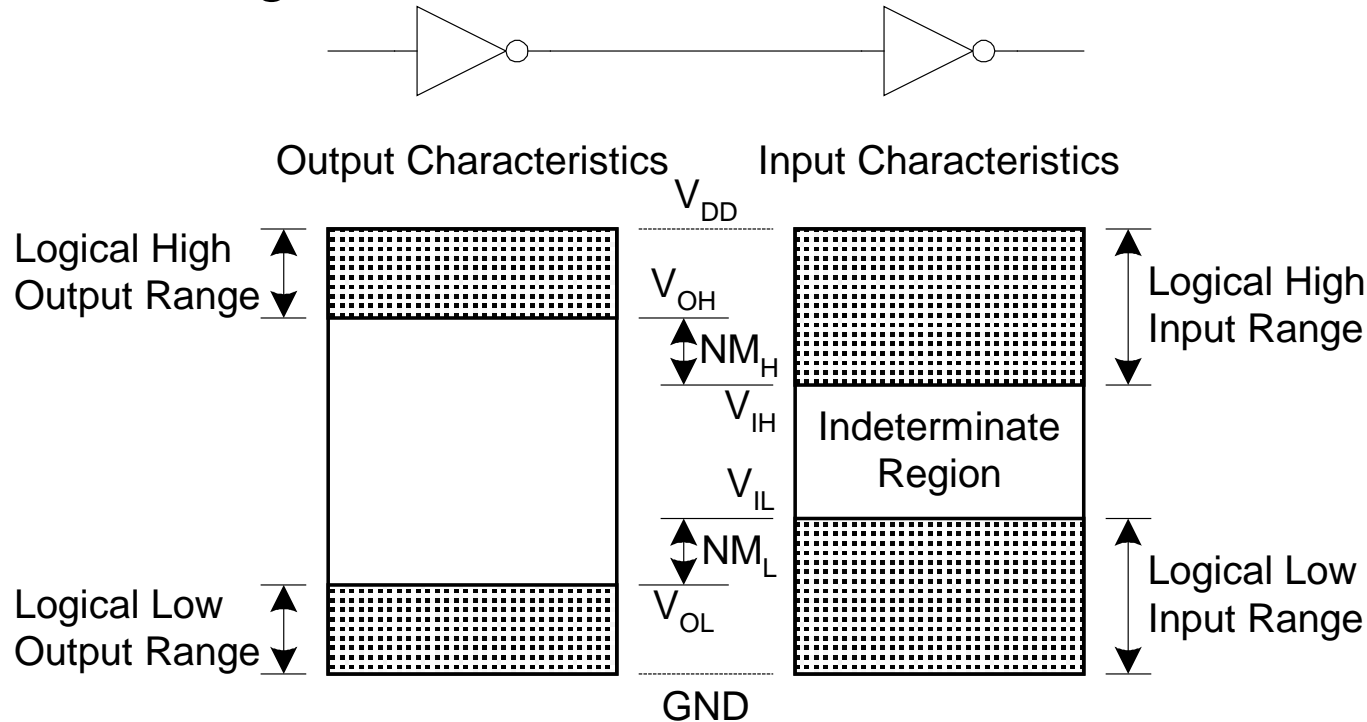


Fig. 2.29

## 2.5. DC transfer (15)

- Unity gain points
  - Two unity gain points
  - $(V_{IL}, V_{OH})$
  - $(V_{IH}, V_{OL})$

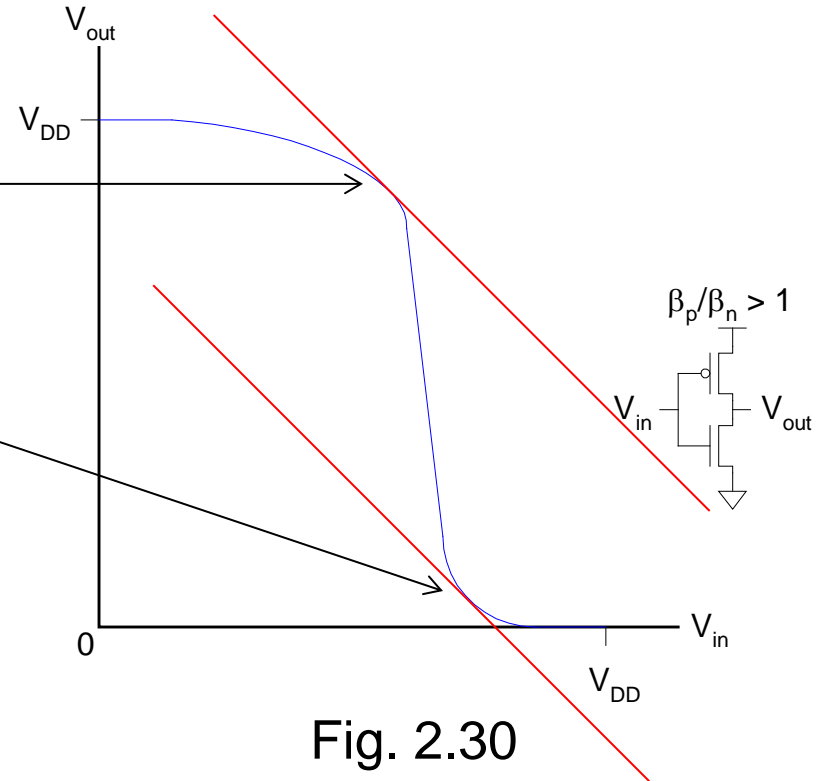


Fig. 2.30

## 2.5. DC transfer (16)

---

- Calculate  $\frac{dV_{out}}{dV_{in}}$  with the channel length modulation

- Assume the NMOS current.

$$I_{dn} = W_n C_{ox} v_{sat-n} (V_{in} - V_{tn}) (1 + \lambda_n V_{out})$$

- Assume the PMOS current.

$$I_{dp} = -W_p C_{ox} v_{sat-p} (V_{in} - V_{DD} - V_{tp}) (1 + \lambda_p (V_{out} - V_{DD}))$$

- What is the determining factor for  $\frac{dV_{out}}{dV_{in}}$ ?

## 2.5. DC transfer (17)

---

- Pass transistor

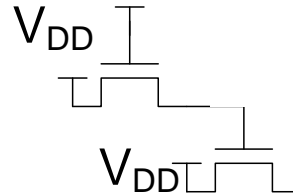
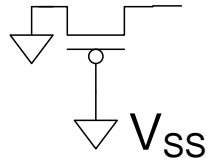
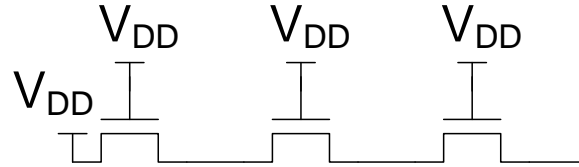
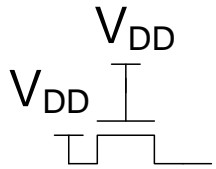


Fig. 2.31

# 4.1. Introduction (1)

---


- Transient response
  - DC analysis:  $V_{out}$  if  $V_{in}$  is a constant
  - Transient analysis:  $V_{out}(t)$  if  $V_{in}(t)$  changes
  - A set of differential equations should be solved.
  - Input is usually considered to be a step or ramp.
    - From 0 to  $V_{DD}$  or vice versa

# 4.1. Introduction (2)

$$V_{in}(t) =$$

$$V_{out}(t < t_0) =$$

$$\frac{dV_{out}(t)}{dt} =$$

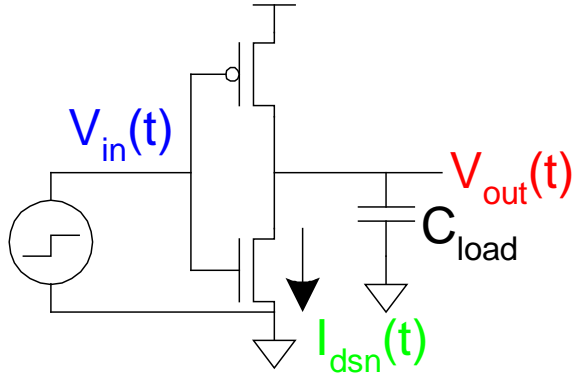

$$I_{dsn}(t) = \begin{cases} t \leq t_0 \\ V_{out} > V_{DD} - V_t \\ V_{out} < V_{DD} - V_t \end{cases}$$

# 4.1. Introduction (3)

- Definitions

- $t_{\text{pdr}}$ : *rising propagation delay*
  - From input to rising output crossing  $V_{\text{DD}}/2$
- $t_{\text{pdf}}$ : *falling propagation delay*
  - From input to falling output crossing  $V_{\text{DD}}/2$
- $t_{\text{pd}}$ : *average propagation delay*,  $t_{\text{pd}} = (t_{\text{pdr}} + t_{\text{pdf}})/2$
- $t_r$ : *rise time*
  - From output crossing  $0.2 V_{\text{DD}}$  to  $0.8 V_{\text{DD}}$
- $t_f$ : *fall time*
  - From output crossing  $0.8 V_{\text{DD}}$  to  $0.2 V_{\text{DD}}$

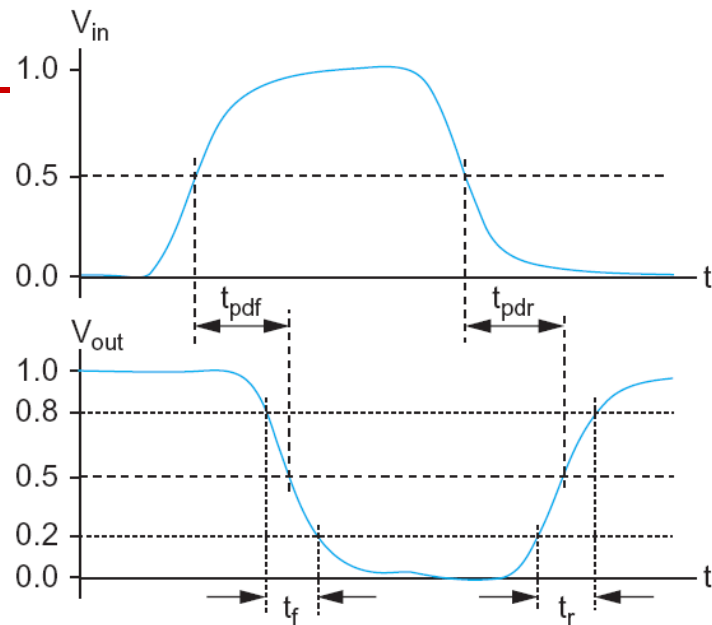


Fig. 4.1