 

DIC L18: Delay (6)

Sung-Min Hong (smhong@gist.ac.kr)

Semiconductor Device Simulation Lab.
School of Electrical Engineering and Computer Science
Gwangju Institute of Science and Technology

4.3. RC delay model (10)

- Layout dependence of capacitance
 - Good layout minimizes the diffusion area.



4.4. Linear delay model (1)

- Delay in a logic gate
 - Express delays in process-independent unit

$$d = \frac{t_{pd}}{\tau} = \frac{t_{pd}}{3RC} \quad \text{Eq. (4.15)}$$

- Delay has two components:

$$d = f + p \quad \text{Eq. (4.20)}$$

- Effort delay

$$f = gh \quad \text{Eq. (4.21)}$$

- Logical effort, g
 - $g \equiv 1$ for inverter

4.4. Linear delay model (2)

- Delay in a logic gate (continued)

- Electrical effort

$$h = \frac{C_{out}}{C_{in}} \quad \text{Eq. (4.22)}$$


- Ratio of output to input capacitance

- Parasitic delay, p

- Represents delay of gate driving no load
 - Set by internal parasitic capacitance


4.4. Linear delay model (3)

- Normalized delay versus fanout

 


 4.4. Linear delay model (4)


- Computing logical effort
 - Logical effort is the ratio of the input capacitance of a gate to the input capacitance of an inverter delivering the same output current.*



$$C_{in} = 3$$
$$g = 3/3$$

 

$$C_{in} = 4$$
$$g = 4/3$$

 

$$C_{in} = 5$$
$$g = 5/3$$

4.4. Linear delay model (5)

- Logical effort of common gates

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		$4/3$	$5/3$	$6/3$	$(n+2)/3$
NOR		$5/3$	$7/3$	$9/3$	$(2n+1)/3$
Tristate / mux	2	2	2	2	2
XOR, XNOR		4, 4	6, 12, 6	8, 16, 16, 8	


4.4. Linear delay model (6)

- Parasitic delay of common gates

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		2	3	4	n
NOR		2	3	4	n
Tristate / mux	2	4	6	8	2n
XOR, XNOR		4	6	8	

4.4. Linear delay model (7)


- Example 4.10

 

- Logical Effort: $g = 1$
- Electrical Effort: $h = 4$
- Parasitic Delay: $p = 1$
- Stage Delay: $d = 5$
- When $\tau = 3RC = 3 \text{ ps}$, the total delay is 15 ps.

4.4. Linear delay model (8)


- Example 4.11

 

- Logical Effort: $g = 1$
- Electrical Effort: $h = 1$
- Parasitic Delay: $p = 1$
- Stage Delay: $d = 2$
- Frequency: $f_{\text{osc}} = 1/(2 \cdot N \cdot d) = 1/4N$

 4.5. Logical effort of paths (1)

- Multistage logic networks
 - Logical effort is independent of size.
 - Electrical effort depends on sizes.



- Some metrics for the path as a whole?

4.5. Logical effort of paths (2)

- Multistage logic networks
 - Logical effort is independent of size.
 - Electrical effort depends on sizes.

Homework#5

- A paper about the Elmore delay will be distributed.
 - Read it!
 - And write a report on it, by summarizing the content.
- Due: October 26, 2019 (Before the lecture starts)
 - Upload your Homework to our GitHub repository.