

---

# DIC L16: Delay (4)

Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Lab.  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology

## 4.3. RC delay model (4)

- Example 4.2

 


Fig. 4.7(b)

 


Fig. 4.7(c)

## 4.3. RC delay model (5)

---

- First-order RC circuit

- Its output voltage follows

$$V_{out}(t) = V_{DD} \exp\left(-\frac{t}{RC}\right) \quad \text{Eq. (4.7)}$$

- Then, the propagation delay becomes

$$t_{pd} = RC \ln 2 \quad \text{Eq. (4.8)}$$

- Second-order RC circuit

$$V_{out}(t) = V_{DD} \frac{\tau_1 e^{-t/\tau_1} - \tau_2 e^{-t/\tau_2}}{\tau_1 - \tau_2} \quad \text{Eq. (4.11)}$$

- How about general RC tree circuits?

## 4.3. RC delay model (6)

---

- Example 4.4
  - Estimate for a “unit” inverter (PMOS width:NMOS width=2:1 & minimum length) driving  $m$  identical “unit” inverters.
  - Effective  $R$  (same for NMOS and PMOS)
  - Capacitance is  $(3+3m)C$ .

$$t_{pd} = (3 + 3m)RC$$

- Example 4.5
  - When the driver is  $w$  times unit size,


$$t_{pd} = \left(3 + 3\frac{m}{w}\right)RC$$

## 4.3. RC delay model (7)

 - Example 4.4
  - A simple single time constant approximation




$$t_{pd} \approx \sum_{\text{nodes } i} R_{i-to-source} C_i \quad \text{Eq. (4.14)}$$

$$= R_1 C_1 + (R_1 + R_2) C_2 + \dots + (R_1 + R_2 + \dots + R_N) C_N$$




# 4.3. RC delay model (8)

- Example 4.7 ( $h$  identical NANDs)

   

$$t_{pdr} = (9 + 5h)RC$$

 

$$\begin{aligned} t_{pdf} &= (3C)\left(\frac{R}{3}\right) + (3C)\left(\frac{R}{3} + \frac{R}{3}\right) + [(9 + 5h)C]\left(\frac{R}{3} + \frac{R}{3} + \frac{R}{3}\right) \\ &= (12 + 5h)RC \end{aligned}$$


## 4.3. RC delay model (9)

---

- Delay components
  - Parasitic delay
    - 9 or 12 RC
    - Independent on load
  - Effort delay
    - $5h$  RC
    - Proportional to load capacitance
 
## 4.3. RC delay model (9)

- Layout dependence of capacitance
  - Good layout minimizes the diffusion area.





## 4.4. Linear delay model (1)

---

- Delay in a logic gate
  - Express delays in process-independent unit

$$d = \frac{t_{pd}}{\tau} = \frac{t_{pd}}{3RC} \quad \text{Eq. (4.15)}$$

- Delay has two components:

$$d = f + p \quad \text{Eq. (4.20)}$$

- Effort delay

$$f = gh \quad \text{Eq. (4.21)}$$

- Logical effort,  $g$ 
    - $g \equiv 1$  for inverter

## 4.4. Linear delay model (2)

---

- Delay in a logic gate (continued)

- Electrical effort

$$h = \frac{C_{out}}{C_{in}} \quad \text{Eq. (4.22)}$$

- Ratio of output to input capacitance

- Parasitic delay,  $p$

- Represents delay of gate driving no load
    - Set by internal parasitic capacitance

## 4.4. Linear delay model (3)

- Normalized delay versus fanout

